


# Computer-Aided VLSI System Design

## Homework 1: Arithmetic Logic Unit

*Graduate Institute of Electronics Engineering, National Taiwan University*




NTU GIEE

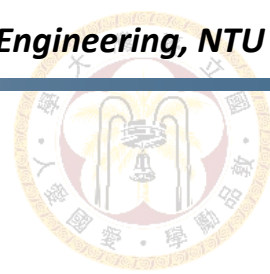

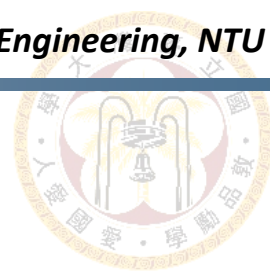
## Goal

- In this homework, you will learn
  - How to read spec
  - How to design ALU with simple operations
  - How to implement various operations by Verilog
  - How to separate combinational circuit and sequential circuit
  - How to write testbench (Optional)




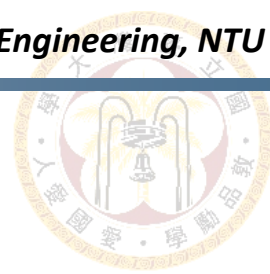
# Introduction

- An arithmetic logic unit (ALU) is one of the components of a computer processor
- ALU performs arithmetic and bit-level logical operations in a computer
- In this homework, you are going to design an ALU with some special instructions




## Block Diagram

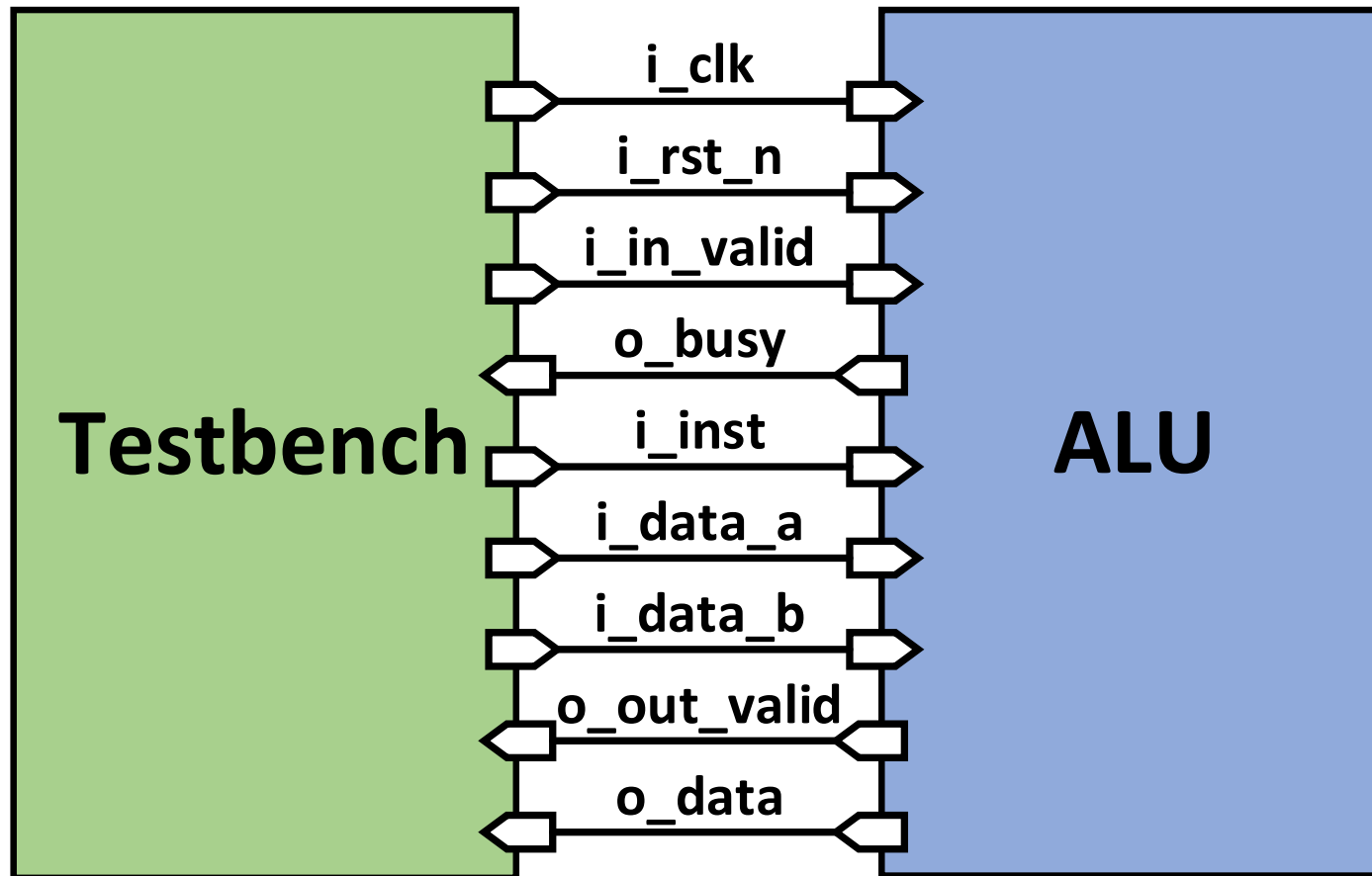

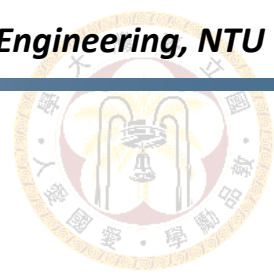


# Input/Output

Signal Name	I/O	Width	Simple Description
i_clk	I	1	Clock signal in the system
i_rst_n	I	1	Active <b>low</b> asynchronous reset
i_in_valid	I	1	The signal is <b>high</b> if input data is ready
o_busy	O	1	Set <b>low</b> if ready for next input data. Set <b>high</b> to pause input sequence.
i_inst	I	4	Instruction for ALU to perform
i_data_a	I	16	Signed input data with 2's complement representation 1. For instructions 0000~0011, fixed point number (6-bit signed integer + 10-bit fraction) 2. For instructions 0100~1001, integer (for instruction 0100, it is unsigned integer!)
i_data_b	I	16	
o_out_valid	O	1	Set <b>high</b> if ready to output result
o_data	O	16	Signed output data with 2's complement representation 1. For instructions 0000~0011, fixed point number (6-bit signed integer + 10-bit fraction) 2. For instructions 0100~1001, integer

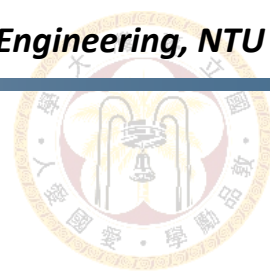

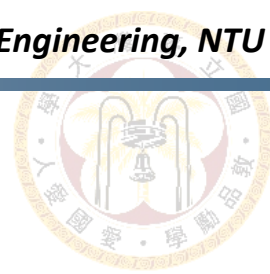
## Specification (1/2)


- Active low asynchronous reset is used only once.
- All inputs are synchronized with the **negative** clock edge.
- All outputs should be synchronized with the **positive** clock edge.
  - Flip-flops should be added before all outputs.
- New pattern (i\_inst, i\_data\_a and i\_data\_b) is ready only when i\_in\_valid is high.
- i\_in\_valid will be randomly pulled high only if o\_busy is low.
- o\_out\_valid should be high for only one cycle for each o\_data.
- The testbench will sample o\_data at **negative** clock edge if o\_out\_valid is high.
- You can raise o\_out\_valid at any moment.


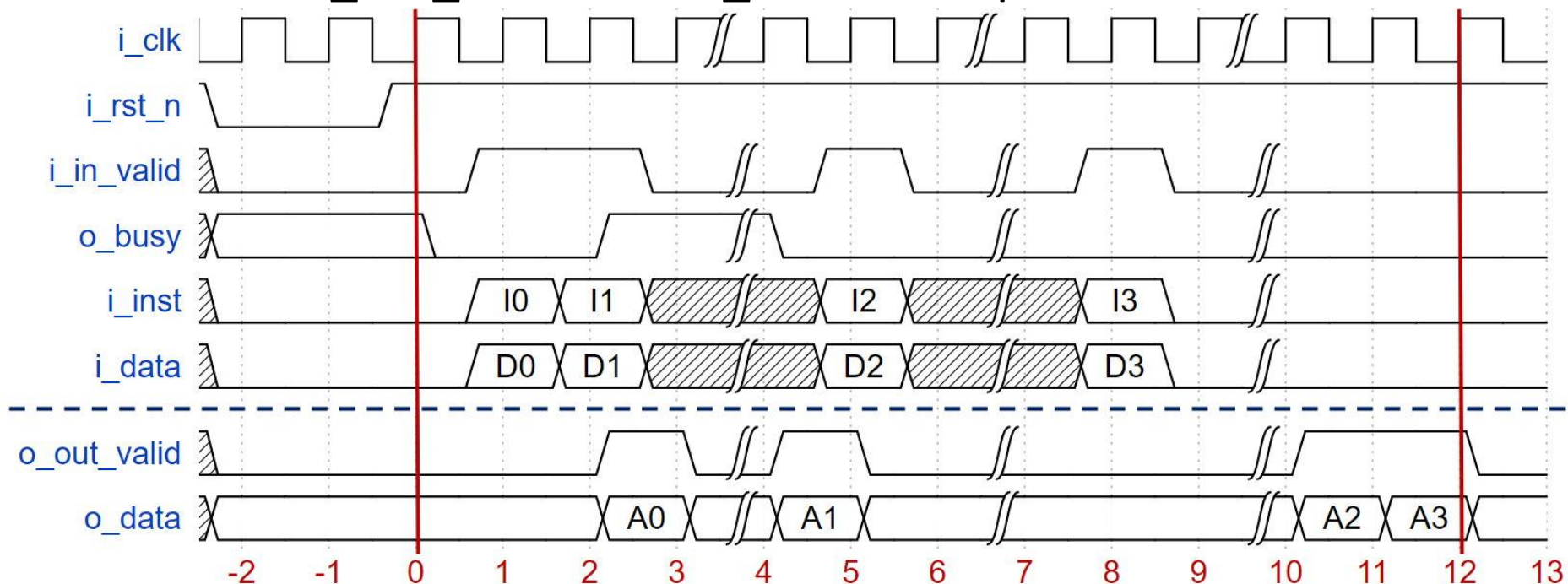
## Specification (2/2)

- $t < 0$ : ALU reset
- $t = 0.5$ :  $o\_busy=0 \rightarrow$  new pattern is presented,  $i\_in\_valid=1$
- $t = 2.5$ :  $o\_busy=1 \rightarrow$  no pattern is presented,  $i\_in\_valid=0$
- $t = 2.5$ :  $o\_out\_valid=1 \rightarrow o\_data$  is sampled




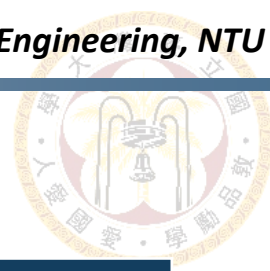

# Instructions


i_inst[3:0]	Operation	Description
4'b0000	Signed Addition	$o\_data = i\_data\_a + i\_data\_b$
4'b0001	Signed Subtraction	$o\_data = i\_data\_a - i\_data\_b$
4'b0010	Signed MAC	$o\_data = i\_data\_a * i\_data\_b + data\_acc_{old}$
4'b0011	Taylor Expansion of Sin Function	$o\_data = \sum_{n=0}^2 \frac{(-1)^n}{(2n+1)!} (i\_data\_a)^{2n+1}$
4'b0100	Binary to Gray Code	Encode the gray code result
4'b0101	LRCW	Encode the CPOP result
4'b0110	Right Rotation	Rotate i_data_a right by i_data_b bits
4'b0111	Count Leading Zeros	Count leading 0's in i_data_a
4'b1000	Reverse Match4	Custom bit-level operation
4'b1001	Matrix Transpose	Transpose an 8*8 matrix




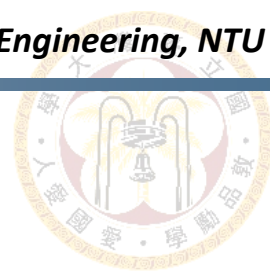
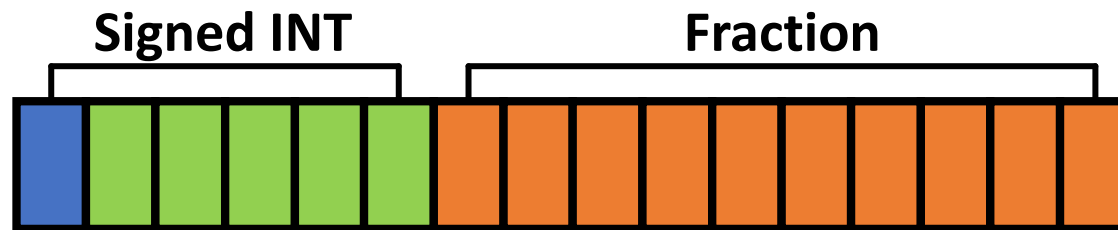
## Fixed-Point Number (1/2)


- Representation used for instruction 0000~0011
  - 6-bit signed integer + 10-bit fraction = 16-bit fixed-point
- Saturation (for instruction 0000~0011)
  - If the final result exceeds the maximum (minimum) representable value of 16-bit representation, use the maximum (minimum) value as output.




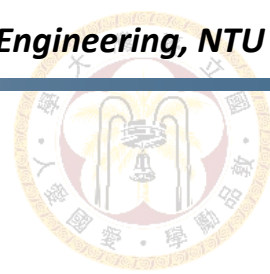
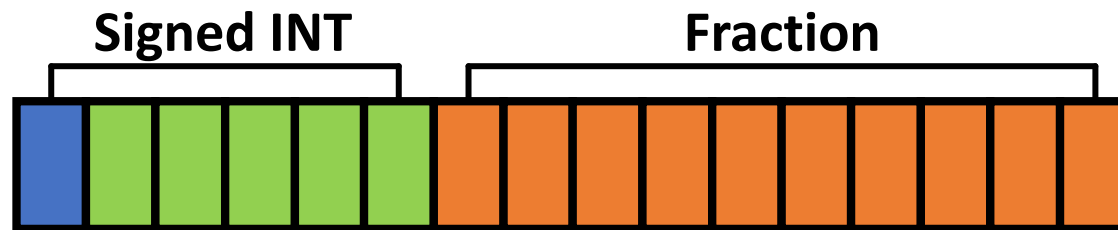
## Fixed-Point Number (2/2)


- Rounding (for instruction 0010 and 0011)
  - The result must be **rounded to the nearest**[2] representable number with 10-bit fraction first
  - For tie-breaking, round half toward positive infinity
  - Then, apply saturation to ensure the final output is a valid 16-bit fixed-point number



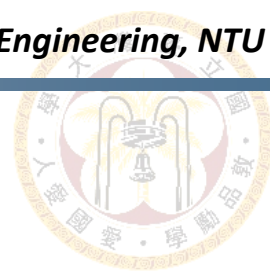
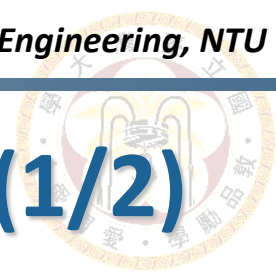
## Signed Add/Sub

- Topic: basic operator, sizing and signing
- i\_data\_a is the first operand
- i\_data\_b is the second operand
- o\_data is the final result
- Saturation must be applied to the output





# Signed Multiplication & Accumulation(1/2)

- Topic: basic operator, sizing and signing
- Implement an accumulator to buffer the intermediate value (initialized to 0 during reset)
- i\_data\_a is the first operand
- i\_data\_b is the second operand
- o\_data is the accumulated result for test
- First, perform the multiply-accumulate (MAC) operation. The accumulated result is then **saturated** to fit within a 36-bit range(16 bits int, 20 bits fraction) before you save it
- Note that any **intermediate value or accumulation value that is going to be accumulated cannot be rounded**
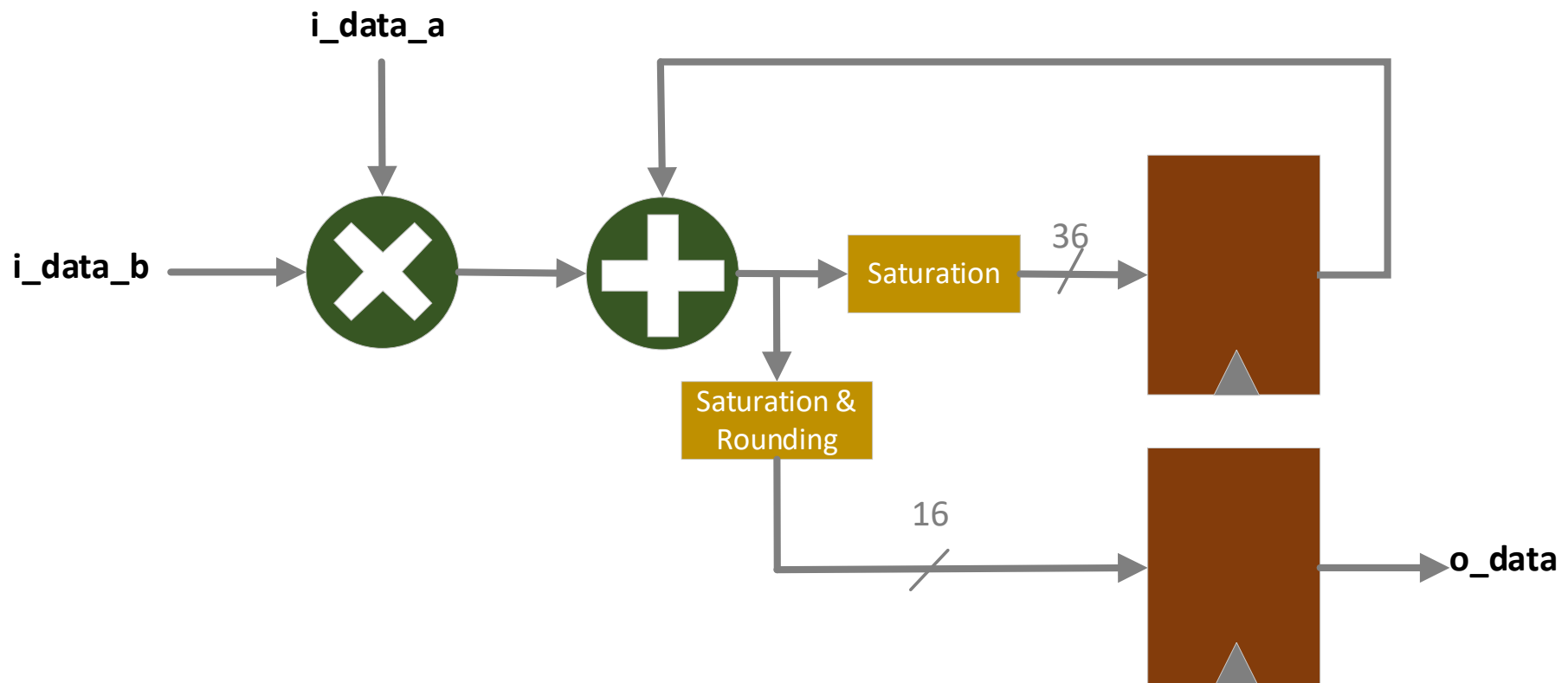
# Signed Multiplication & Accumulation(2/2)

- Rounding and saturation (to 16 bits) must be applied to the accumulation result before you output it



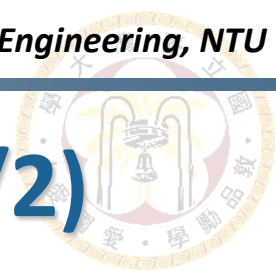


# Taylor Expansion of Sin Function (1/2)

- Topic: linear approximation, constant division
- Implement the sin function by Taylor expansion
- The input is guaranteed to be in the range of  $-1.0 \leq i\_data\_a \leq 1.0$
- Use the following **linear approximation** to compute  $\sin(i\_data\_a)$ :


$$\sin(i\_data\_a) \cong \sum_{n=0}^2 \frac{(-1)^n}{(2n+1)!} (i\_data\_a)^{2n+1}$$

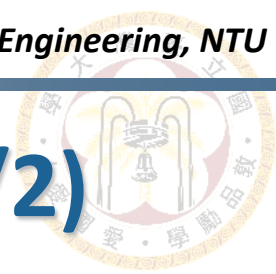- You are not allowed to use the division operator (/) in Verilog code.
- The output (after rounding and saturation) must be **exactly the same as the golden** for any input value in the required range



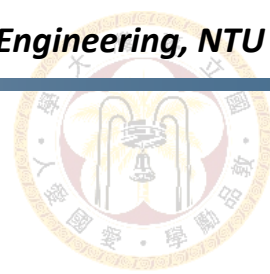
# Taylor Expansion of Sin Function (2/2)

- Topic: linear approximation, constant division
- Fixed-point constant division algorithms
  - Long division → Too slow
  - DesignWare → Banned in this homework
  - **By multiplication?**
- Rule:
  - You **have to** find the two **16 bits fixed points (6 bits int, 10 bits fraction)** that are **closest to the reciprocal** in the provided equation, respectively
  - Do **multiplication** instead of division
- Apply rounding and saturation only to the final output data



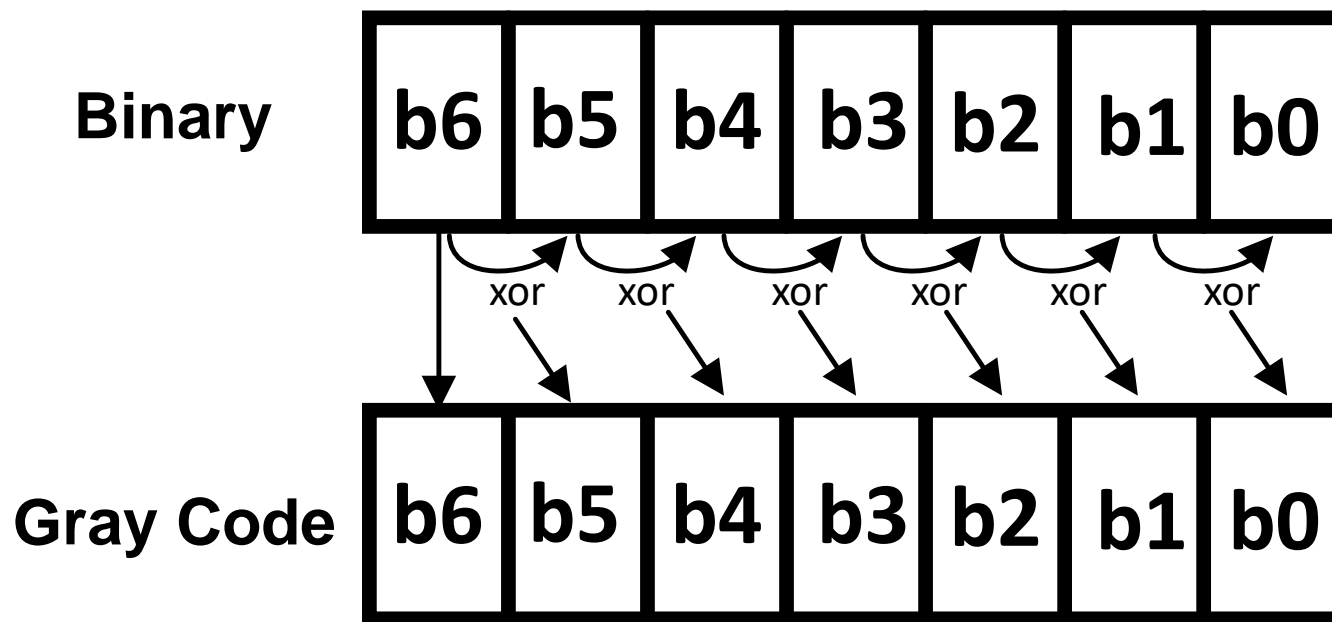
## Binary to Gray Code, LRCW(1/2)

- Topic: bit-level operation, shifting
- Binary to Gray Code
- 7-bit example:





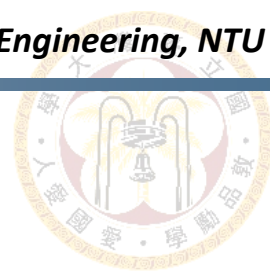


## Binary to Gray Code, LRCW(2/2)


- For LRCW, you need to implement an unary encoding of the popcnt by Left rotation and complement-on-warp [5].
- View `i_data_a` as the bit mask.
- View `i_data_b` as the initial value.
- Calculate the **CPOP** of the `i_data_a` first, and encode it by LRCW, which is initialized by `i_data_b`.
  - The number of the set bits determines the iteration times.
- 4-bit example:

`i_data_a: 0001`

**CPOP(a) = 1**


`i_data_b: 0011`

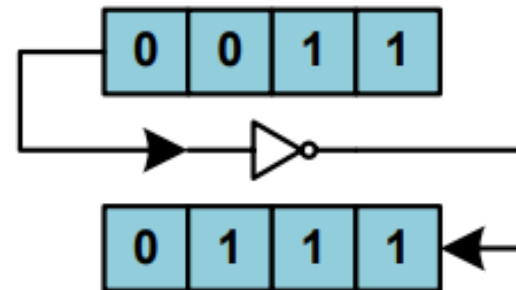

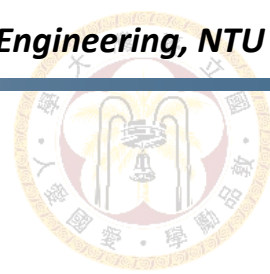

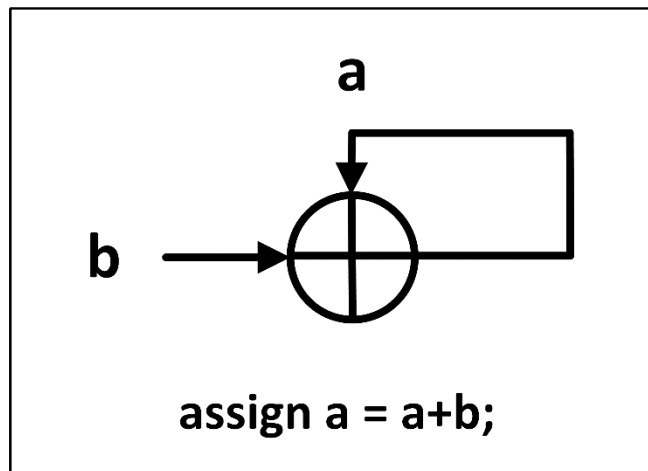
## CPOP

- Count the number of set bits.
- For example, if  $a = 8'b0010\_0001$ , then  $CPOP(a)=2$ .
- Note you have to **avoid** the **combinational loop**, where static timing analysis (STA) cannot be applied.






An error example

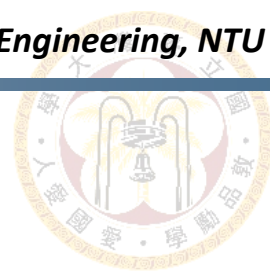
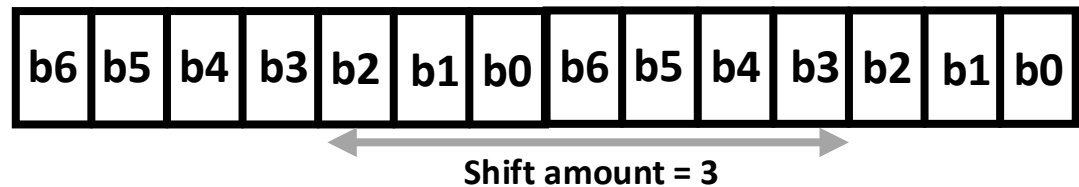 
## Right Rotation

- Topic: vector concatenation, vector part select (optional)
- Right rotation, also called right circular shift, inserts the bit that got shifted out at one end back to the other end
- `i_data_a` is the original pattern
- `i_data_b` is the shift amount, and is guaranteed to be from 0 to 16 (inclusive)




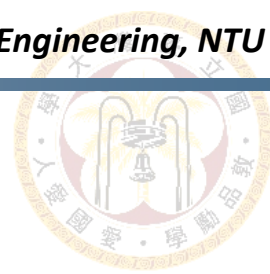


# Count Leading Zeros

- Topic: for loop, combinational loop, generate block (optional)
- Count the number of consecutive 0's from MSB
- For example, if  $a = 8'b0010\_0000$ , then  $CLZ(a)=2$
- It is recommended to use **for loops** instead of hand crafting everything
- Be aware of combinational loop, where static timing analysis (STA) cannot be applied

0010\_0000  
MSB →

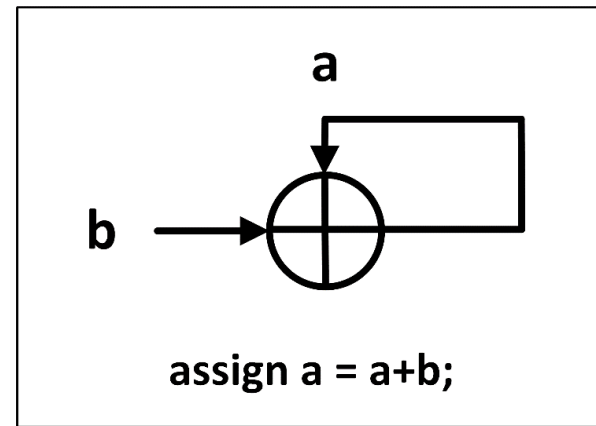

An error example

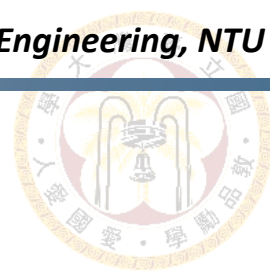



## Reverse Match4

- Topic: for loop, vector part select, generate block (optional)
- This is a custom bit-level operation that matches 4 bits of `i_data_a` and `i_data_b` at a time in reverse order

$$o\_data[i] = \begin{cases} (i\_data\_a[i + 3 : i] == i\_data\_b[15 - i : 12 - i]), & i = 0 \sim 12 \\ 0, & i = 13 \sim 15 \end{cases}$$


- For example:

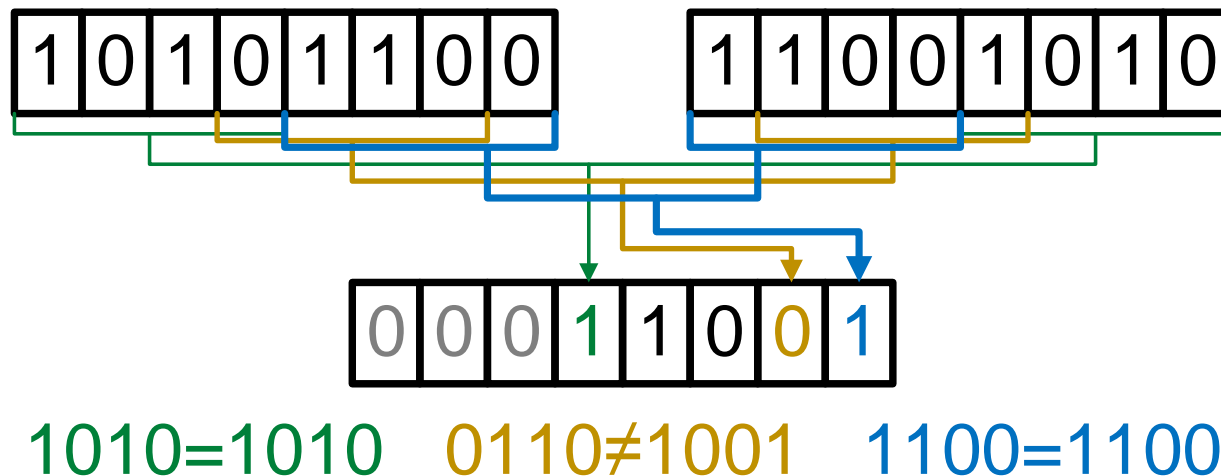

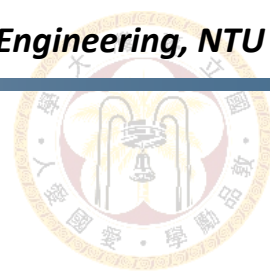
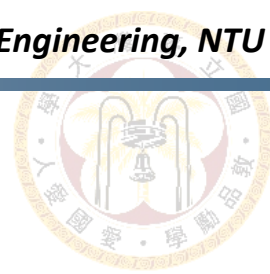
## Matrix Transpose (1/3)

- Topic: for loop, vector part select, vector array
- This instruction implement an  $8 \times 8$  matrix transpose, with each entry in the matrix being 2 bits
- Thus, this operation requires collecting 8 cycles of valid input data. These cycles may arrive non-consecutively, but the entire 8-cycle transfer is guaranteed to complete before the next instruction is issued
- The input `i_data_a` represents one column vector at a time, which is provided in sequential order from column 0 through column 7



## Matrix Transpose (2/3)

- The input `i_data_a` is partitioned into 2-bit segments. The most significant 2-bit segment is mapped to row 0 of the matrix, continuing down to the least significant 2-bit segment, which is mapped to row 7


`i_data_a = 11_01_00_01_10_01_11_10`  
(in the very first valid cycle)

8*8 Matrix									
	Col 0								
Row 0	11								Col 0 Col 1 Col 2 Col 3 Col 4 Col 5 Col 6 Col 7
Row 1	01								Row 0 11 01 00 01 10 01 11 10
Row 2	00								
Row 3	01								
Row 4	10								
Row 5	01								
Row 6	11								
Row 7	10								

After Transpose




	Col 0	Col 1	Col 2	Col 3	Col 4	Col 5	Col 6	Col 7
Row 0	11	01	00	01	10	01	11	10

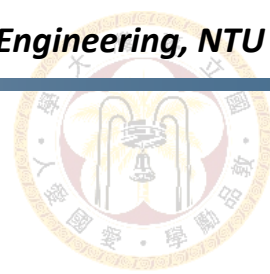

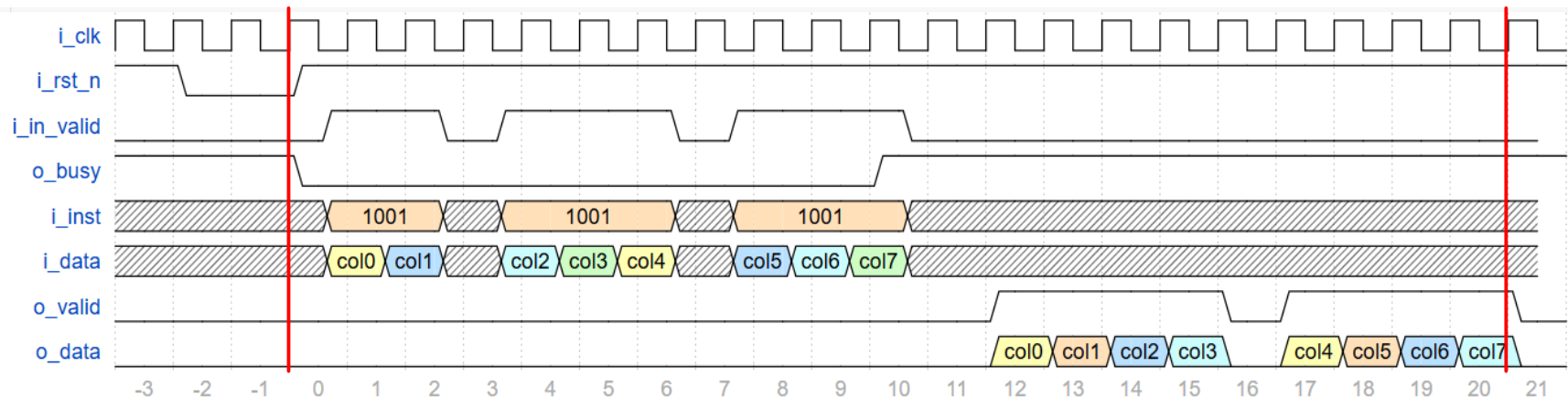
## Matrix Transpose (3/3)

- The output data should be transmitted over 8 cycles. The `o_valid` signal must be asserted during each cycle that contains valid output data of the transposed matrix
- The valid output data should be packed into a column vector using the same format as the input vector `i_data_a`
- All valid results for the current matrix transpose operation must be output before the results from the **subsequent instruction** are transmitted






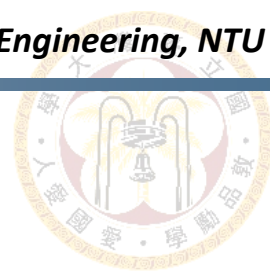

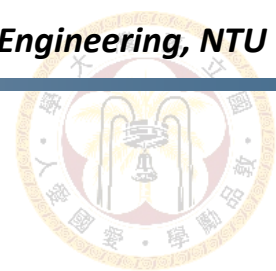
## Other Requirements

- Check your code with SpyGlass
  - Goal setup: lint\_rtl and lint\_rtl\_enhanced
  - List of waivable errors will be updated on NTU Cool
  - If you encounter any error that seems waivable, check with TA on NTU Cool
  
- You **CANNOT** implement any operation by look up tables (the scaling factors of reciprocal in instruction 0011 are allowed)
  
- You are **NOT** allowed to use DesignWare


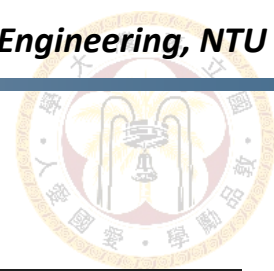
## alu.v

```
module alu #(  
    parameter INST_W = 4,  
    parameter INT_W  = 6,  
    parameter FRAC_W = 10,  
    parameter DATA_W = INT_W + FRAC_W  
)(  
    input                i_clk,  
    input                i_rst_n,  
  
    input                i_in_valid,  
    output               o_busy,  
    input                [INST_W-1:0] i_inst,  
    input signed [DATA_W-1:0] i_data_a,  
    input signed [DATA_W-1:0] i_data_b,  
  
    output               o_out_valid,  
    output               [DATA_W-1:0] o_data  
);
```




# testbench.v

```
`timescale 1ns/10ps
`define PERIOD      10.0
`define MAX_CYCLE 100000
`define RST_DELAY 2.0


`define SEQ_LEN 60
`ifdef I0
    `define IDATA  "../00_TESTBED/pattern/INST0_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST0_O.dat"
    `define PAT_LEN 40
`elsif I1
    `define IDATA  "../00_TESTBED/pattern/INST1_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST1_O.dat"
    `define PAT_LEN 40
`elsif I2
    `define IDATA  "../00_TESTBED/pattern/INST2_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST2_O.dat"
    `define PAT_LEN 40
`elsif I3
    `define IDATA  "../00_TESTBED/pattern/INST3_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST3_O.dat"
    `define PAT_LEN 40
`elsif I4
    `define IDATA  "../00_TESTBED/pattern/INST4_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST4_O.dat"
    `define PAT_LEN 40
`elsif I5
```

```
`elsif I5
    `define IDATA  "../00_TESTBED/pattern/INST5_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST5_O.dat"
    `define PAT_LEN 40
`elsif I6
    `define IDATA  "../00_TESTBED/pattern/INST6_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST6_O.dat"
    `define PAT_LEN 40
`elsif I7
    `define IDATA  "../00_TESTBED/pattern/INST7_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST7_O.dat"
    `define PAT_LEN 40
`elsif I8
    `define IDATA  "../00_TESTBED/pattern/INST8_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST8_O.dat"
    `define PAT_LEN 40
`elsif I9
    `define IDATA  "../00_TESTBED/pattern/INST9_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST9_O.dat"
    `define PAT_LEN 40
`else
    `define IDATA  "../00_TESTBED/pattern/INST0_I.dat"
    `define ODATA  "../00_TESTBED/pattern/INST0_O.dat"
    `define PAT_LEN 40
`endif
```

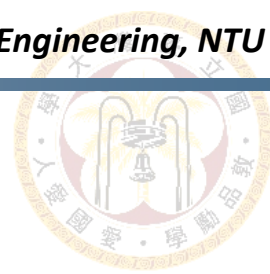
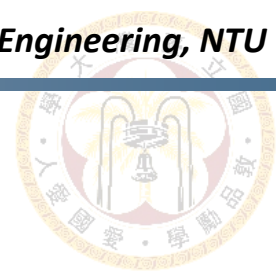
# Commands

- `./01_run <arg1>`
  - `vcs -full64 -R -f rtl.f +v2k -sverilog -debug_access+all +define+$1`
  - For example: `./01_run I0` (arg1 = I0~I9)
- `./99_clean`
  - Remove all temporary files
- Before you execute the shell script, **change the permission of the file by** `chmod +x <script filename>`



## Pattern (Input Data)


**i\_inst**

**i\_data\_a**

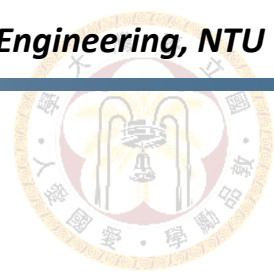**i\_data\_b**

```
000001010110011000010011101000100011
000000001101010000110001001110101011
000001101010010000111011111000101101
000000101111100011110010011111110000
000000010010110111011001010100001010
000001001101011110110001110110111110
000001011101100000110010011010001111
000001111001001101010011011111100110
000010000000001000100110000001111000
000001011010000101110111011110001010
000000011010010111100100000111001100
```






# Pattern (Golden Output)

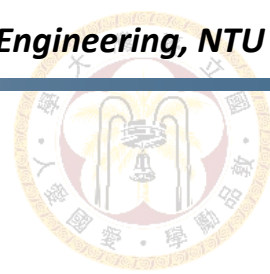**o\_data**

```
01111111111111111111
0010000011101110
0010100001110000
0101011101111111
1010011111100111
0110101100111001
0111111111111111
0111111111111111
1110000010011010
0111111111111111
0101110000101010
```




# Submission

- Create a folder named **studentID\_hw1** and follow the hierarchy below (\*.sv is allowed if you use SystemVerilog)

```
r13943000_hw1
├── 01_RTL
│   ├── alu.v
│   ├── xxx.v (other verilog files you wrote)
│   └── rtl.f
```

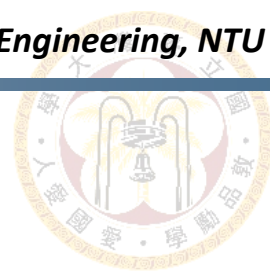- Pack the folder **studentID\_hw1** into a **tar file** named **studentID\_hw1\_vk.tar** ( $k$  is the number of version,  $k = 1, 2, \dots$ )
  - **tar -cvf studentID\_hw1\_vk.tar studentID\_hw1**
  - Use **lowercase** for all the letters. (e.g. r13943000\_hw1\_v1.tar)
  - Pack the folder on IC Design LAB server to avoid OS related problems
- Submit to NTU Cool



# Grading Policy (1/3)


- Grading command

- `vcs -full64 -R -f rtl.f +v2k -sverilog -debug_access+all +define+$1`

- Released patterns: **70%**


i_inst[3:0]	Operation	Score
4'b0000	Signed Addition	5%
4'b0001	Signed Subtraction	5%
4'b0010	Signed MAC	10%
4'b0011	Taylor Expansion of Sin Function	10%
4'b0100	Binary to Gray Code	5%
4'b0101	LRCW	5%
4'b0110	Right Rotation	5%
4'b0111	Count Leading Zeros	8%
4'b1000	Reverse Match4	8%
4'b1001	Matrix Transpose	9%



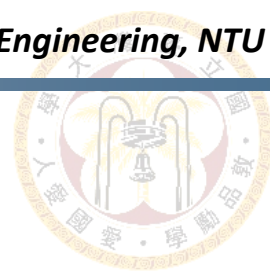

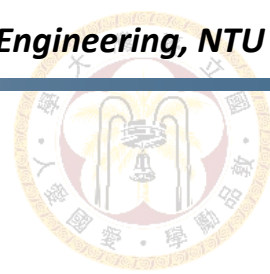
## Grading Policy (2/3)

- Grading command
  - `vcs -full64 -R -f rtl.f +v2k -sverilog -debug_access+all +define+$1`
- Hidden patterns: **30%**
  - Mixture of all instructions
- SpyGlass check with error: **-20%**
  - Check **Discussion** on NTU Cool for waivable errors
- All your code has to be synthesizable or you will get **0 point**
- Lose **5 points** for any incorrect naming or format
  - Make sure all your files can be correctly unpacked and executed on IC Design LAB server


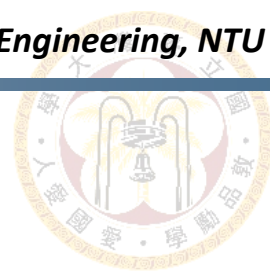
## Grading Policy (3/3)

- **Deadline:** 2025/09/30 13:59:59 (UTC+8)
- Late submissions are not accepted
  - Any submission after the deadline will receive 0 points
- File corrections after the deadline should be avoided
  - Corrections for the folder name, file name, file hierarchy cause 5-point deduction
- The TA will grade your submissions by using scripts
- **No plagiarism**
  - **Plagiarism in any form, including copying from online sources, is strictly prohibited**




# Discussion

- **NTU Cool Discussion Forum**

- For any questions not related to assignment answers or privacy concerns, please use the NTU Cool discussion forum.
- **TAs will prioritize answering questions on the NTU Cool discussion forum**

- **Email: r13943123@ntu.edu.tw**

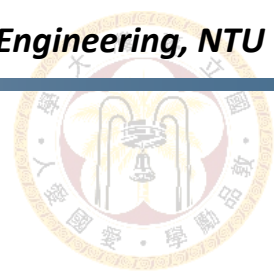- Title should start with **[CVSD 2025 Fall HW1]**
- Email with wrong title will be moved to trash automatically



# Discussion

☰ 電腦輔助積體電路系統設計 (EEE5022) > 討論 > [HW1]Discussion

課程內容

課程資訊

公告

作業

討論

Gradescope

成績

設定

## [HW1]Discussion

所有班別

HW1相關問題在此討論，並請以下列格式發問，方便助教按照每個問題回答

1. 問題一

2. 問題二

...

另外，若需要截圖，請勿把自己的code截圖或code文字上傳，變成大家的參考答案，若違反將扣本次作業總分10分。

祝同學們學習順心


by TA

[提醒]

1. ...

2. ...

3. ...

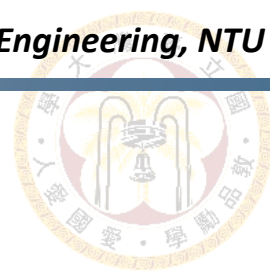

# References

- [1] Reference for fixed-point representation
  - [Fixed-Point Representation](#)
- [2] Reference for rounding to the nearest
  - [Rounding - MATLAB & Simulink](#)
- [3] Reference for Taylor Expansion function
  - [Taylor series - Wikipedia](#)
- [4] Reference for reciprocal multiplication
  - [Reciprocal Multiplication](#)
- [5] Reference for LRCW
  - [Comparing fast implementations of bit permutation instructions](#)